 


## Binary to Gray RTL design

**Modeling:** data flow model

**Schematic:** (logic level diagram)




**Input ports :** Bin[3];


**Output ports :** Gray[3];

**Nets :** NA

**Waveforms :**

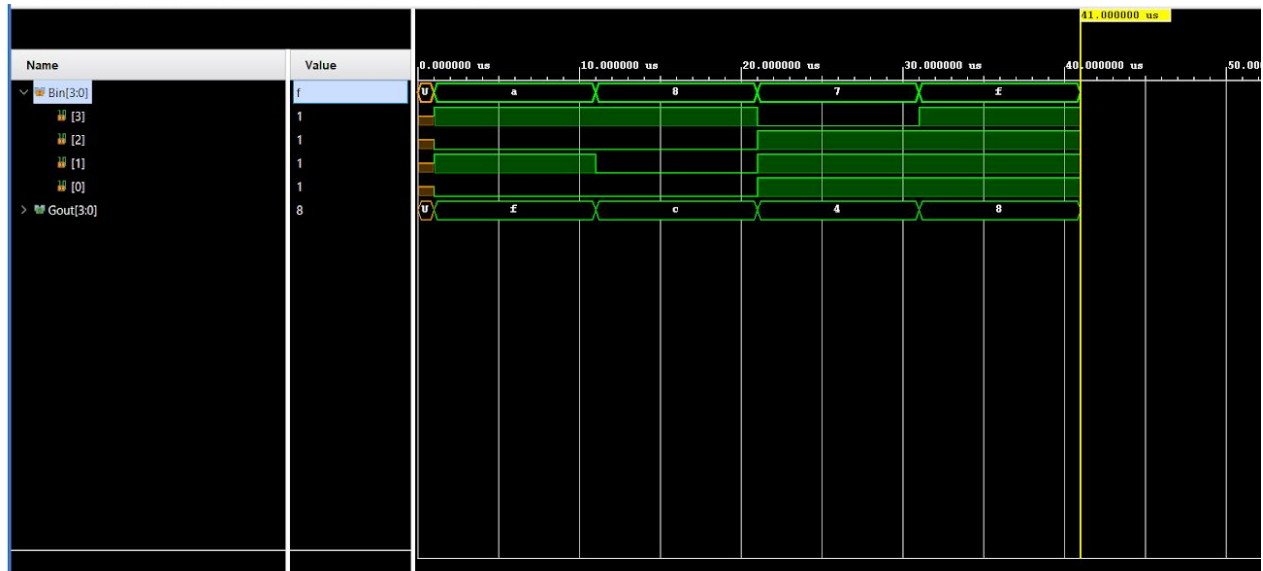

### RTL analysis Schematic:

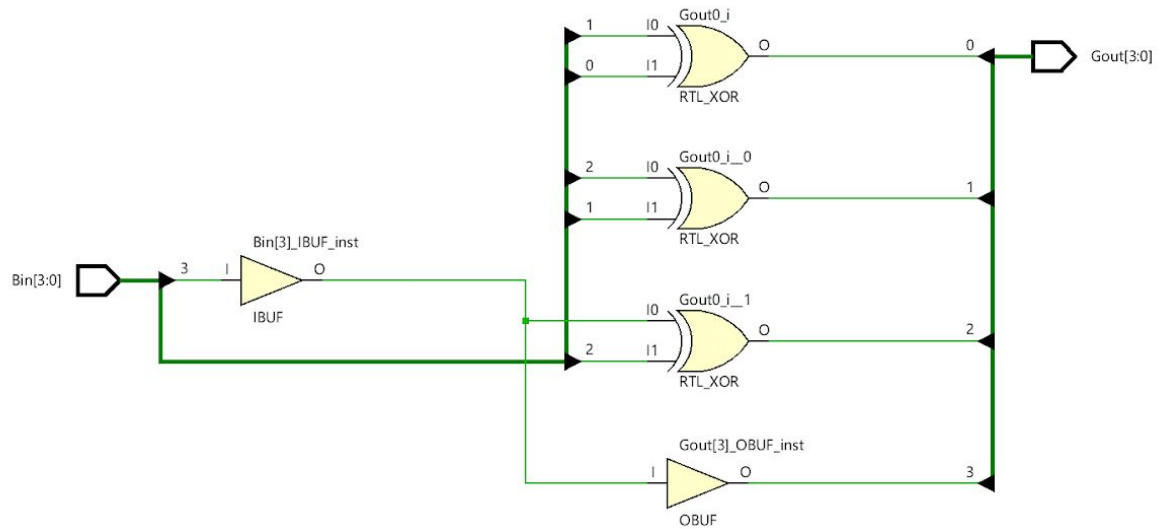

### Synthesis schematic:

