 


Modeling: data flow model

Schematic: (logic level diagram)




Input ports : A,B, Cin


Output ports : S, Cout

Nets : t1 (A xor B), t2 (t1 and Cin), t3 (b and a)

Waveforms :

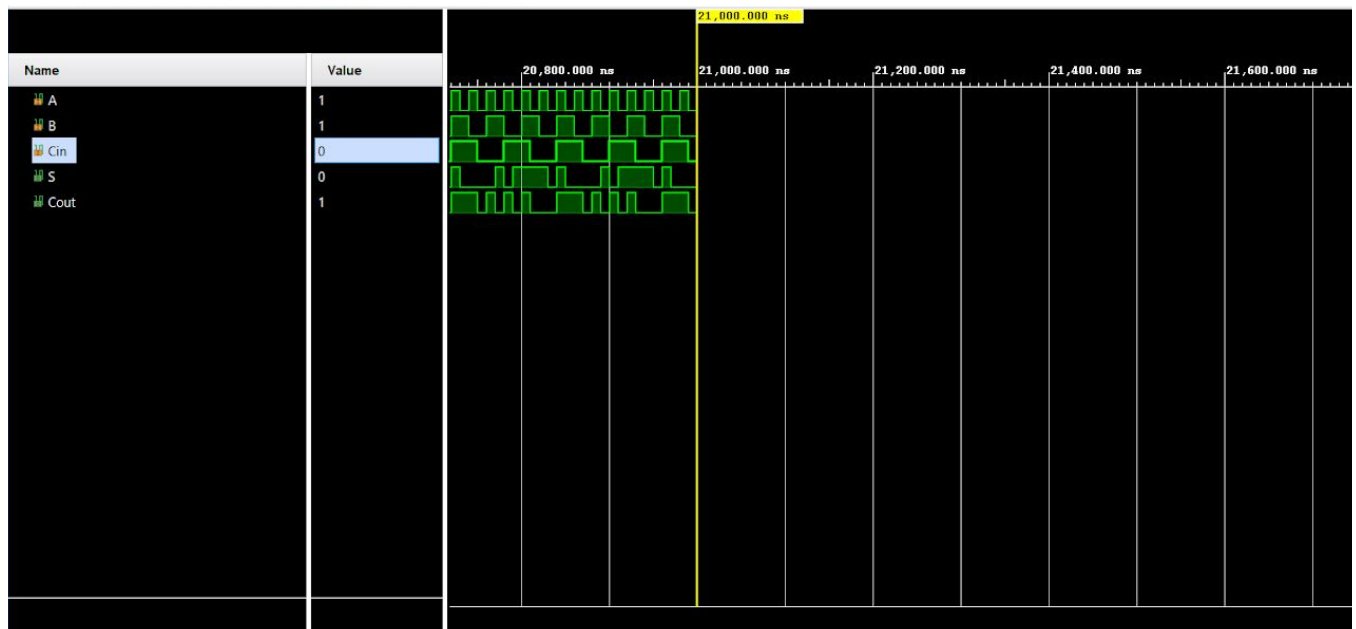

RTL analysis Schematic:

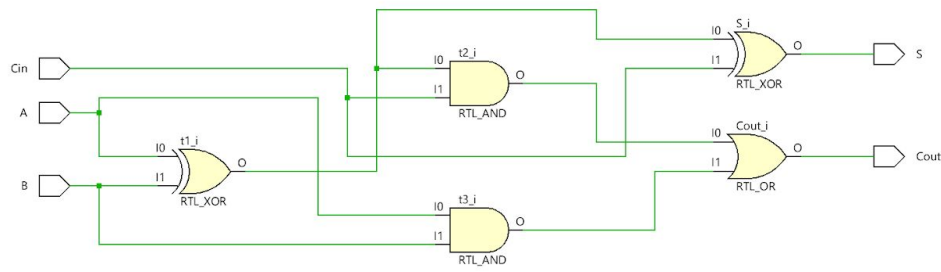

Synthesis schematic:

