 


**STRUCTURAL MODELLING**  
**MUX 4 : 1 USING 2:1 MUX**

RTL schematic :



**Code:**

```
entity MUX_21 is
Port (
a,b,sel : in std_logic;
y      : out std_logic
);
end MUX_21;
```

architecture Behavioral of MUX\_21 is

```
begin
process
begin
if(sel = '1') then
y <= a;
else
y <= b;
end if;
end process;
```

end Behavioral;

-----end-----

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity MUX\_41 is

Port (

a,b,c,d : in std\_logic;

sel : in std\_logic\_vector ( 1 downto 0);

y : out std\_logic

);

end MUX\_41;

architecture Behavioral of MUX\_41 is

component

MUX\_21 is

Port (

a,b,sel : in std\_logic;

y : out std\_logic

);

end component;

signal t1: std\_logic;

signal t2: std\_logic;

begin


M1: MUX\_21 port map(a=>a,b=>b,sel=>sel(1),y=>t1);

M2: MUX\_21 port map(a=>c,b=>d,sel=>sel(1),y=>t2);

M3: MUX\_21 port map(a=>t1,b=>t2,sel=>sel(0),y=>y);


end Behavioral;

## RTL schematic:

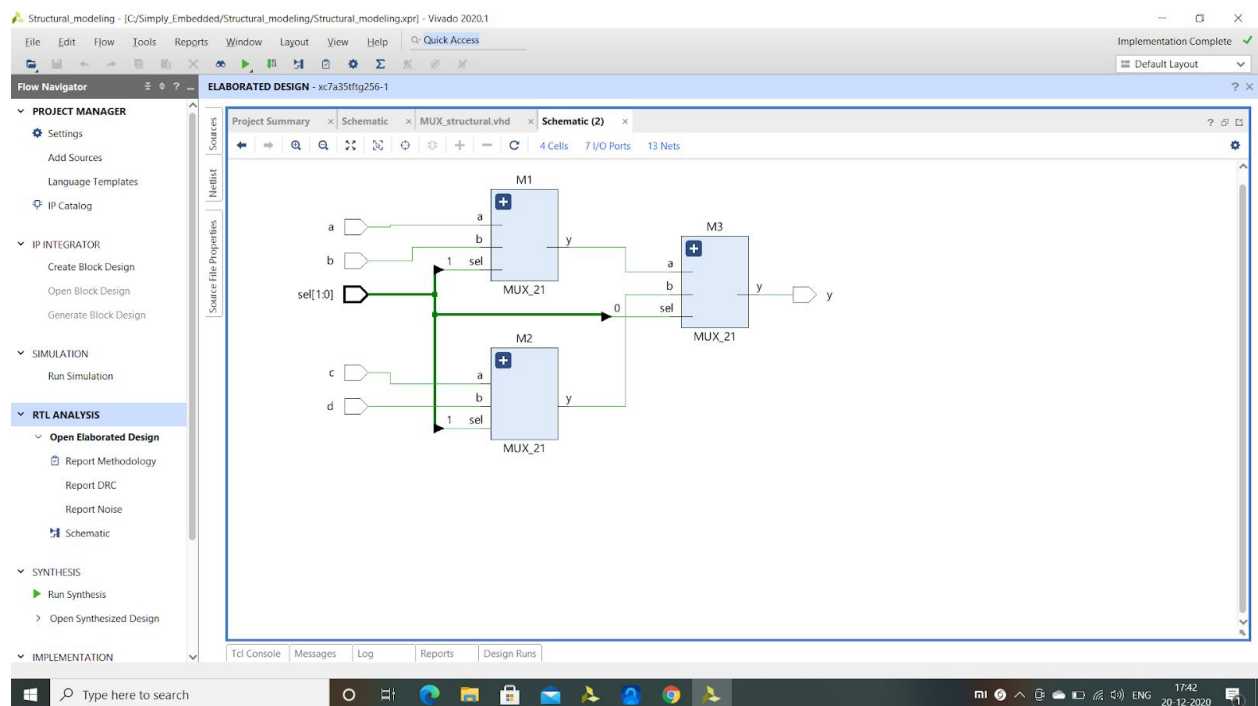

## FULL ADDER USING HALF ADDER

### Schematic:

 

**Code:**

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity halfadder is
```

```
Port (
```

```
a,b : in std_logic;
```

```
c,s : out std_logic
```

```
);
```

```
end halfadder;
```

```
architecture Behavioral of halfadder is
```

```
begin
```

```
c <= a and b;
```

```
s <= a xor b;
```

```
end Behavioral;
```

```
-----
```

```
-----
```

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity fulladder is
```

```
Port (
```

```
a,b,cin : in std_logic;
```

```
cout,s   : out std_logic
```

```
);
```

```
end fulladder;
```

```
architecture Behavioral of fulladder is
```

```
component halfadder is
```

```
Port (
```

```
a,b: in std_logic;
```

```
c,s : out std_logic
```

```
);
```

```
end component;
```

```
signal t1 : std_logic;
```


```
signal t2 : std_logic;
```

```


signal t3 : std_logic;
begin
S1 : halfadder port map(a=>a,b=>b,c=>t3,s=>t1);
S2 : halfadder port map(a=>cin,b=>t1,c=>t2,s=>s);
cout <= t2 or t3;
cout <= t2 or t3;
end Behavioral;

```

## RTL schematic:

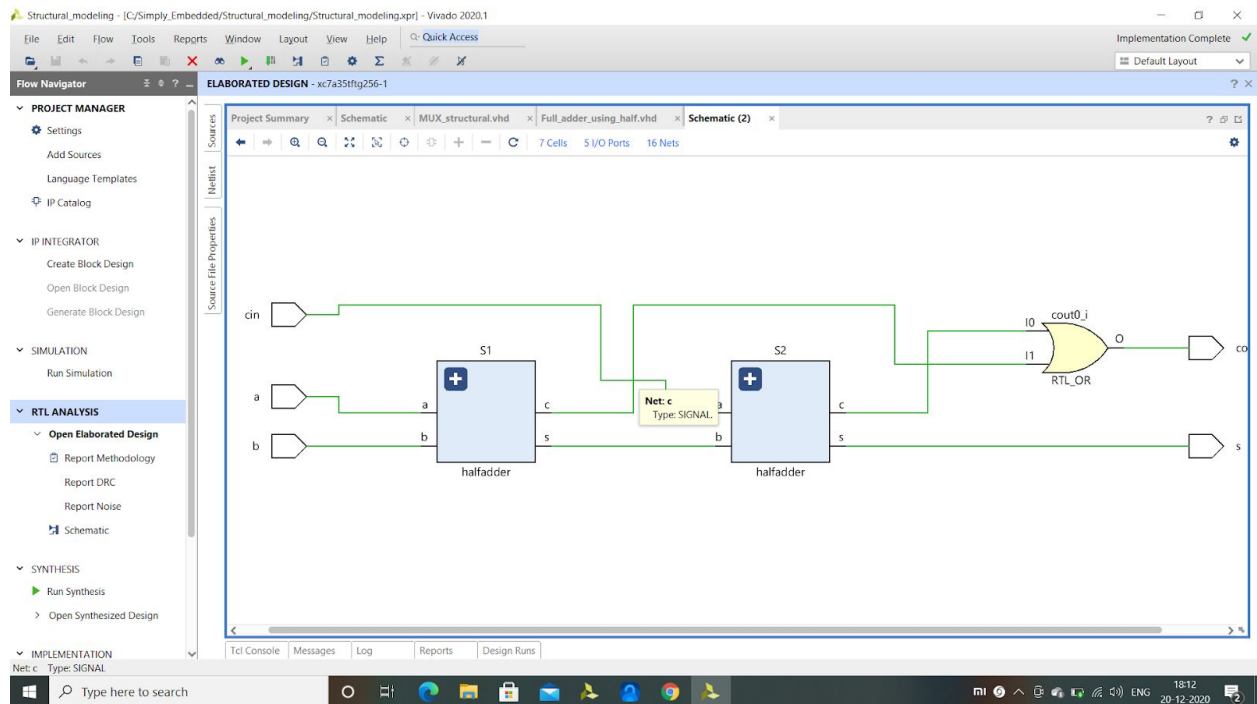

## Four bit adder Schematic:

 

### Code:

```
entity halfadder1 is
Port (
a,b : in std_logic;
c,s : out std_logic

);
end halfadder1;
```

architecture Behavioral of halfadder1 is

```
begin
c <= a and b;
s <= a xor b;
```

```
end Behavioral;
```

```
-----
-----
```

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity fulladder1 is
Port (
a,b,cin : in std_logic;
cout,s   : out std_logic
```

```
);  
end fulladder1;
```

architecture Behavioral of fulladder1 is  
component halfadder1 is

```
Port (  
a,b: in std_logic;  
c,s : out std_logic
```

```
);  
end component;  
signal t1 : std_logic;  
signal t2 : std_logic;  
signal t3 : std_logic;  
begin  
S1 : halfadder1 port map(a=>a,b=>b,c=>t3,s=>t1);  
S2 : halfadder1 port map(a=>cin,b=>t1,c=>t2,s=>s);  
cout <= t2 or t3;  
cout <= t2 or t3;  
end Behavioral;
```

```
-----  
-----
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity fourbitadder is  
Port (  
a,b : in std_logic_vector (3 downto 0);  
sum  : out std_logic_vector (3 downto 0);  
cout : out std_logic
```

```
);  
end fourbitadder;
```

architecture Behavioral of fourbitadder is  
component fulladder1 is

```
Port (  
a,b,cin : in std_logic;  
cout,s  : out std_logic
```

```
);  
end component;  
signal cin,c0,c1,c2 : std_logic:='0';  
begin
```

```

FA1 : fulladder1 port map(a=>a(0),b=>b(0),cin=>cin,cout=>c0,s=>sum(0));
FA2 : fulladder1 port map(a=>a(1),b=>b(1),cin=>c0,cout=>c1,s=>sum(1));
FA3 : fulladder1 port map(a=>a(2),b=>b(2),cin=>c1,cout=>c2,s=>sum(2));
FA4 : fulladder1 port map(a=>a(3),b=>b(3),cin=>c2,cout=>cout,s=>sum(3));

```

end Behavioral;

## RTL schematic:

