

## Conditional statement example Selected Concurrent Statement

**Modeling:** Behavioural modeling

**Entity** : 4:1 mux;


**Input ports** : A,B,C,D. Sel

**Output ports** : Y


**Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Selected is
Port (
a,b,c,d : in std_logic;
sel : in bit_vector(1 downto 0);
Y : out std_logic
);
end Selected;
architecture Behavioral of Selected is
begin
with sel select
Y <= a when "00",
    b when "01",
    c when "10",
    d when "11";
end Behavioral;
```

**RTL analysis Schematic:**

 

**Synthesis schematic:**

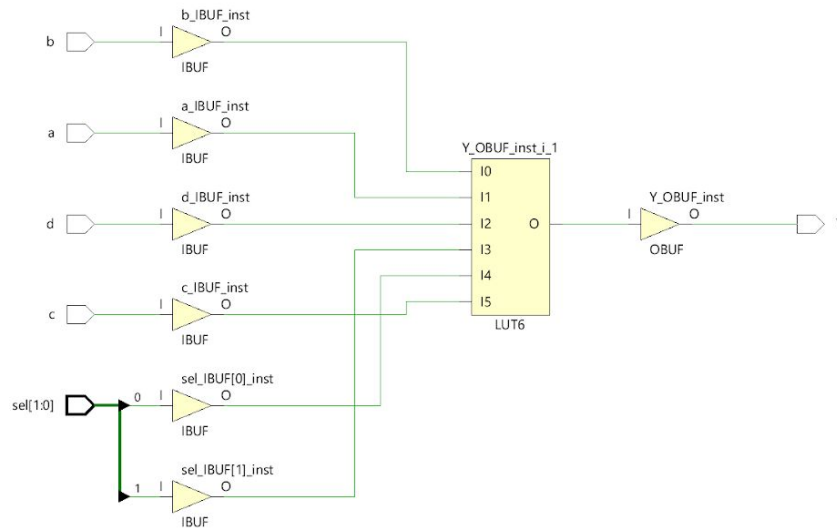

### Conditional concurrent statement (with latch)

**Modeling:** Behavioural modeling

**Entity** : 3:1 mux;

**Input ports** : a,b,c,sel1,sel2

**Output ports** : Y

**Waveforms** :

**Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
```


```
entity Conditional2 is
Port (
a,b,c,d: in std_logic;
sel : in std_logic_vector(1 downto 0);
Y : out std_logic
);
end Conditional2;
```

architecture Behavioral of Conditional2 is


```
begin
Y <= a when sel = "00" else
  b when sel = "01" else
```

end Behavioral;

### RTL analysis Schematic:

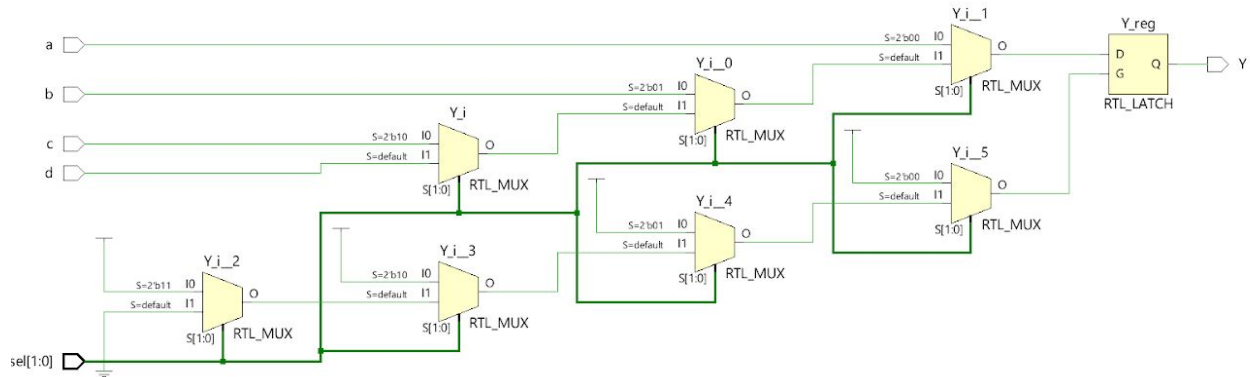

**Synthesis schematic:**

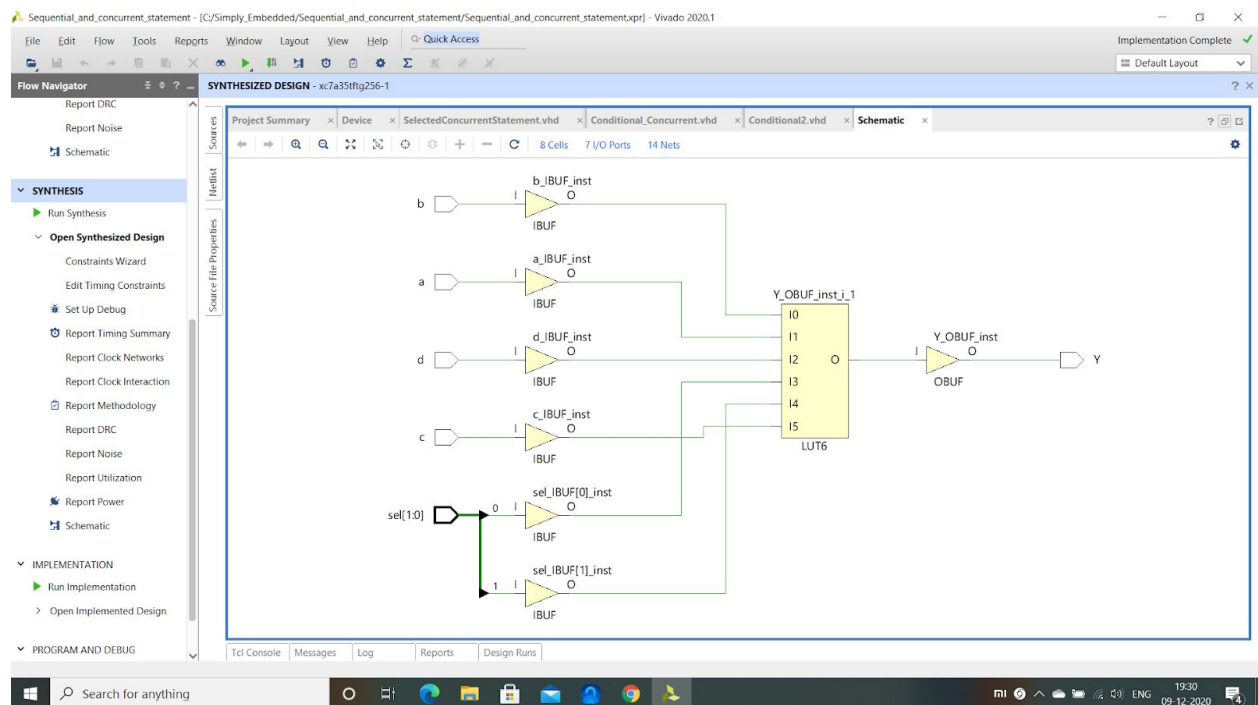

### Conditional concurrent statement (without latch)

**Modeling:** Behavioural modeling

**Entity** : 3:1 mux;

**Input ports** : a,b,c,sel1,sel2

**Output ports** : Y

**Code:**

entity Conditional2 is

Port (

a,b,c,d: in std\_logic;

sel : in std\_logic\_vector(1 downto 0);

Y : out std\_logic

);

end Conditional2;

architecture Behavioral of Conditional2 is

begin

Y <= a when sel = "00" else

b when sel = "01" else


c when sel = "10" else

d when sel = "11" else

'0';

end Behavioral;

**RTL analysis Schematic:**

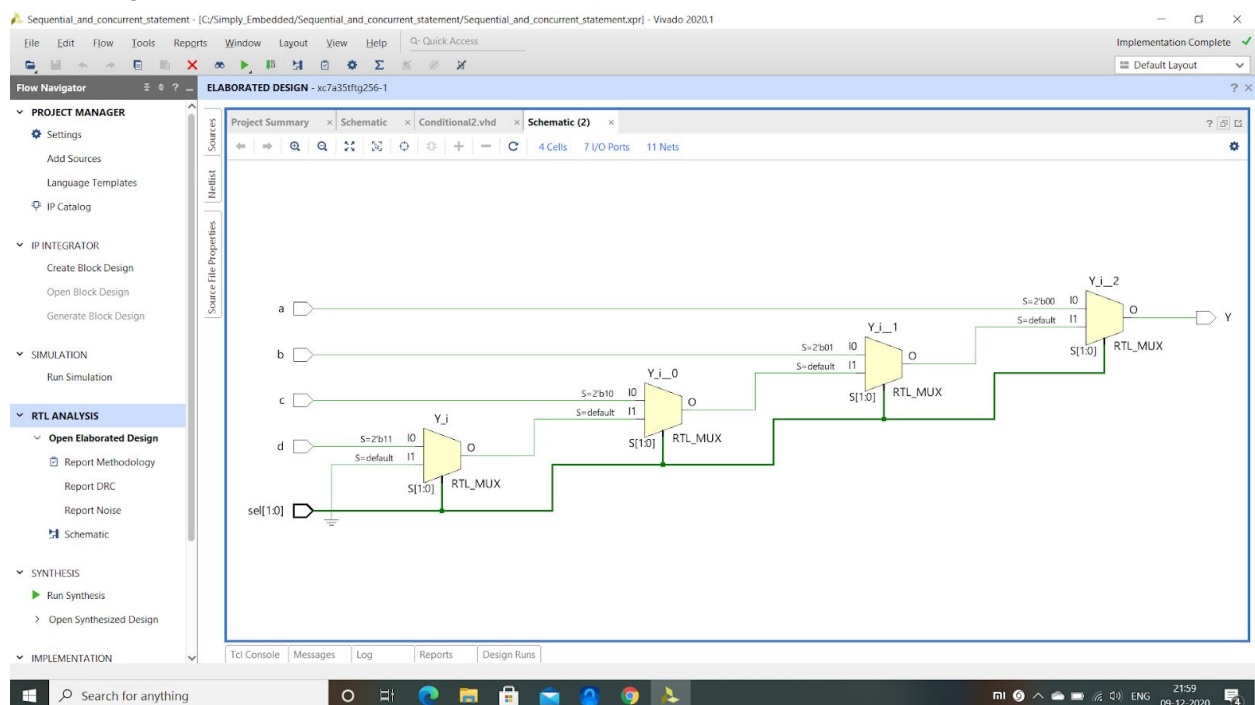

**Note: formation of latch is undesirable a statement similar to 'default' was added to avoid latch formation**

**Synthesis schematic:**

